

EE 140/240A discussion 2

Eric Chang

Outline

- Circuit Analysis vs Modeling
- Biasing Scheme
- When to approximate?
- Analysis Example


Stages of Circuit Analysis

1. Small Signal Model + KCL/KVL (EE 105).
 - The Golden Standard; gives you the 100% correct answer.
 - Too slow to do, no intuition of how the circuit works.
 - Fallback option on exams/interviews.
2. Inspection Analysis (EE 140).
 - Memorize solution to common circuit configuration.
 - It is recommended to memorize exact formula in case assumption break.
 - Offers some circuit intuition.
3. Current Flow Intuition.
 - Completely intuition driven.
 - Comes only after thousands of practices.

Circuit Analysis vs Modeling


- Circuit analysis is given a circuit configuration, calculate its properties (gain, input impedance, etc.)
- Modeling is given a (possibly unknown) circuit, find the simplest equivalent circuit that captures all the properties of interest.
- Good models can simplify complex circuits and provide valuable insights into how it works.

1 Port Circuit Modeling

 

- Thévenin's/Norton's Theorem: Any **linear** circuit can be modeling as a voltage/current source in series/parallel to a resistor.
- Proof: Because we know it's linear, We must have $V_1 = V_{bias} - Z_{eq}I_1$, or $I_1 = I_{bias} + V_1/Z_{eq}$

2 Port Circuit Modeling

 

- We now have 4 variables, V_1 , V_2 , I_1 , and I_2 .
- Since it's linear, we can write:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

– Why is this? **Superposition Principle**

- A 2 port circuit can be completely described by 4 parameters.

2 Port Circuit Modeling

- We can derive:


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

- For a transistor, we see that $y_{11} = \infty$, $y_{12} = 0$, $y_{21} = g_m$, and $y_{22} = 1/r_o$.
- For more information, Wikipedia has a good article.
 - Will revisit 2-port networks for feedback analysis near the end of the semester.


Biasing

 - Circuit Design is 95% biasing - Ali Niknejad.
- How to bias the gate of a transistor?
- Following picture is ideal, but restrict previous stage to work with sub-optimal bias point.




Biasing

 - Doesn't work: input DC bias voltage overrides resistor divider network.
- We want to disconnect the input at DC.



Biasing

 
- Add a capacitor.
- $Z_C = \frac{1}{j\omega C}$
 - at DC ($\omega = 0$), infinite impedance -> open.
 - At frequencies for which $\omega C \gg 1$, 0 impedance -> short.
 - Pick C such that $\omega C \gg 1$ for all frequencies of interest.



When to approximate?

- Engineers are not mathematicians; we are lazy and only do minimum amount of work.
- Each specification usually comes with an error tolerance; as long as your approximation is within error tolerance, you're fine.
- In this class, unless otherwise stated, 10% error is acceptable.
- **ALWAYS** double check if assumption is valid!

Analysis Example

 


- Find bias currents, input/output resistance, and voltage gain. Ignore r_o , and $V_{BE(on)} = 0.7\text{ V}$, $\beta_0 = 200$.

DC operating point


- $V_{E1} = 5 - V_{BE(on)} = 4.3V$
- $V_{E2} = V_{E1} - V_{BE(on)} = 3.6V$
- $I_{Q2} = \frac{V_{E2}}{50} - \frac{V_{E1} - V_{E2}}{1000} = 71.3mA$
- $g_{m2} = \frac{I_{Q2}}{V_T} = 2.74S, r_{\pi2} = \frac{\beta_0}{g_{m2}} = 73\Omega,$
 $i_{b2} = \frac{I_{Q2}}{\beta_0} = 357\mu A$
- $I_{Q1} = \frac{V_{E1} - V_{E2}}{1000} + i_{b2} = 1.06mA,$
 $g_{m1} = \frac{I_{Q1}}{V_T} = 40.8mS, r_{\pi1} = \frac{\beta_0}{g_{m1}} = 4.9k\Omega$

Input impedance

 


- We can put Q2 in a black box, and since it only has 1 port, we can replace it by an equivalent resistance.
- $1k\Omega$ transistor in parallel with $r_{\pi2} = 73\Omega$, so we can ignore it.
 - Circuit in red box is effectively an emitter degenerated npn transistor.

Input impedance

 

- Using inspection formulas:
 - $R_{eq2} = r_{\pi 2} + (\beta_0 + 1)50 = 10.1\text{k}\Omega$
 - $r_{in} = r_{\pi 1} + (\beta_0 + 1)R_{eq2} = 2.04\text{M}\Omega$

Output Impedance

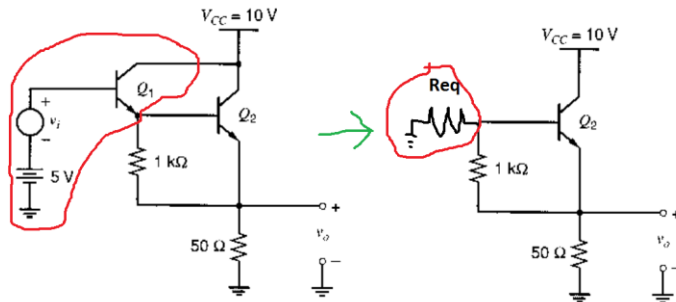

- Similarly, we can blackbox Q1 and find equivalent resistance.
- Inspection formula gives:
 - $R_{eq1} = \frac{1}{g_{m1}} = 24.5\Omega$.
 - $r_{e2} = \frac{1}{g_{m2}} + \frac{R_{eq}}{\beta_0 + 1} = 0.49\Omega$
 - $r_{out} = \left(\frac{1}{r_{e2}} + \frac{1}{50} \right)^{-1} = 0.49\Omega$

Gain

- Blackboxing also works for computing the gain of each stage.

$$\bullet A_{v1} = \frac{R_{eq2}}{R_{eq2} + r_{e1}} = \frac{R_{eq2}}{R_{eq2} + R_{eq1}} = \frac{10100}{10100 + 24.5} \approx 1$$

$$\bullet A_{v2} = \frac{50}{50 + r_{e2}} = \frac{50}{50 + 0.48} \approx 1$$

$$\bullet A_v = A_{v1} A_{v2} = 1$$